



Department of Electrical & Computer Engineering

ENCS4370 - Computer Architecture

## **Design and Implementation of a Multi-Cycle Processor for MIPS Instructions**

Prepared By:

Saja Shareef 1200901

Shereen Ibdah 1200373

Hamza Awashra 1201619

Date: January 22, 2024

## Table of Contents

Table of Figures: .....	4
Table of Tables .....	5
<b>Abstract</b> .....	6
<b>Introduction:</b> .....	7
RISC Overview: .....	7
Multi-Cycle Processors: .....	7
<b>1. Instruction Fetch (IF):</b> .....	7
<b>2. Instruction Decode (ID):</b> .....	7
<b>3. Execution (EX):</b> .....	7
4. Memory Access (MEM): .....	8
5. Write Back (WB): .....	8
<b>Design Specifications and Implementation,</b> .....	8
Processor Properties: .....	8
Instruction Types and Formats .....	9
<b>R-Type (Register Type):</b> .....	9
<b>I-Type (Immediate Type):</b> .....	9
<b>J-Type (Jump Type):</b> .....	9
<b>S-Type (Stack):</b> .....	10
Instruction Set .....	11
<b>Data Path Design and details and description</b> .....	12
Instruction and Data memory .....	16
ALU:.....	19
Register File .....	20
Extenders .....	22
Multiplexers .....	23
Instruction Register and Program counter.....	24
<b>State diagram</b> .....	25
DATA PATH .....	26
<b>Design Procedure</b> .....	27
Main Control Signals .....	27
Main Control Signals.....	27
Main Control Truth Table.....	30

Logic Equation for Main Control (control_unit module).....	31
PC Control Unit.....	32
<b>Testing</b> .....	33
Sample Instructions for testing.....	33
<b>PUSH Instruction</b> .....	33
<b>POP Instruction</b> .....	34
<b>ADD Instruction</b> .....	35
<b>ANDI Instruction</b> .....	35
<b>SW Instruction</b> .....	36
<b>LW Instruction</b> .....	37
<b>LW.POI</b> .....	37
<b>BGT Instruction</b> .....	38
<b>CALL Instruction</b> .....	39
<b>RET Instruction</b> .....	39
Team Work .....	41
Conclusion .....	42

## Table of Figures:

Figure 1:R-Type Format .....	9
Figure 2:I-Type Format.....	9
Figure 3: J-Type Format .....	10
Figure 4: S-Type Format.....	10
Figure 5:Instruction Set.....	11
Figure 6 instruction and data memory .....	16
Figure 7code and test bench for Data Memory.....	17
Figure 8waveform simulation for Data Memory .....	17
Figure 9code and test bench for instruction memory.....	18
Figure 10 test bench for instruction memory .....	18
Figure 11 ALU .....	19
Figure 12 code and test bench for ALU.....	19
Figure 13 ALU test-bench .....	20
Figure 14 Register file .....	20
Figure 15 code and test bench for Register File .....	21
Figure 16 Register File wave form .....	21
Figure 17 Extender.....	22
Figure 18 code and test bench for extender .....	22
Figure 19 simulation for extender.....	23
Figure 20Multiplexers.....	23
Figure 21 IR and PC .....	24
Figure 22: state diagram.....	25
Figure 23: Data Path .....	26
Figure 24: Control Unit.....	27
Figure 25: control unit module .....	31
Figure 26: test bench (control unit ).....	31
Figure 27: PC Source Signal Block .....	32
Figure 28:instructions in memory .....	33
Figure 29 push.....	33
Figure 30 POP.....	34
Figure 31 ADD .....	35
Figure 32 ANDI .....	36
Figure 33 SW .....	36
Figure 34 LW .....	37
Figure 35 LW.POI .....	38
Figure 36 BGT .....	38
Figure 37 CALL.....	39
Figure 38 RET.....	40

## Table of Tables

Table 1: Main Control Signals.....	29
Table 2: Main Control Truth Table.....	30
Table 3: PC_TABLE.....	32

## Abstract

This report explores the creation and application of a Multi-Cycle Processor following a specified instruction set. We designed it by carefully looking at each instruction and identifying the essential parts it requires. The next step involved constructing these parts and figuring out how to control them. To ensure everything works as expected, we tested each component separately, connected these components, tested each instruction separately, and also tested instructions that depend on each other.

## **Introduction:**

In this project, the aim is to design, model, and simulate a MIPS Multi-Cycle Processor using Verilog HDL. The approach taken involves breaking down the processor into sub-modules, each of which is individually designed, coded, and tested. Once these sub-modules are verified as fully functional, they are integrated into a structural module to constitute the complete processor.

## **RISC Overview:**

RISC, or Reduced Instruction Set Computing, prioritizes enhanced CPU performance through a streamlined instruction set. With fixed-length instructions, identical registers, simple addressing, and one-cycle execution, RISC processors deliver speed and cost-effectiveness, widely adopted in the industry.

## **Multi-Cycle Processors:**

Multi-cycle processors divide instruction execution into stages, allowing efficient processing of complex instructions. Unlike single-cycle counterparts, they enable varied instruction completion times, optimizing overall performance and accommodating diverse instruction types.

In a multi-cycle processor, each instruction undergoes several stages, with each stage completing within a single clock cycle. These stages include:

### **1. Instruction Fetch (IF):**

Fetching the instruction from memory using the program counter (PC) and updating the PC for the next instruction.

### **2. Instruction Decode (ID):**

Decoding the fetched instruction to identify the operation and fetching any necessary operands or data from registers.

### **3. Execution (EX):**

Performing the actual operation specified by the instruction, which may involve arithmetic calculations, logical operations, or address computations.

#### **4. Memory Access (MEM):**

Accessing memory, such as loading or storing data, if the instruction requires it. This stage involves reading from or writing to memory.

#### **5. Write Back (WB):**

Writing the results of the previous stage back to the appropriate register(s), and updating the register file with the computed values.

### **Design Specifications and Implementation,**

#### **Processor Properties:**

1. **Instruction and Word Size:** Instructions and words are uniformly set at 32 bits for consistent data handling.
2. **General-Purpose Registers:** Equipped with 16 versatile 32-bit general-purpose registers, labeled from R0 to R15, offering a storage for varied data.
3. **Special Purpose Registers:** Features a 32-bit program counter (PC) for efficient program sequencing.
4. **Stack Management:** Employs a 32-bit stack pointer (SP), visible to the programmer, directing to the topmost empty element of the Last in First Out (LIFO) stack. This stack records crucial information like return addresses and register values during function calls.
5. **Program Memory Layout:** Divided into three segments: Static data, Code, and Stack. The Stack, operating on a LIFO basis, incorporates explicit instructions enabling push/pop operations, facilitating the storage of essential data.
6. **Physical Memories:** Utilizes two separate physical memories—one for instructions and the other for data. The data memory caters to both the static data segment and the stack segment.
7. **Instruction Types:** Supports four instruction types: R-type, I-type, J-type, and S-type, accommodating diverse program needs.
8. **Memory Structure:** Adopts word-addressable memory, enhancing efficiency in data manipulation and retrieval.
9. **ALU Signal Generation:** Utilizes the Arithmetic Logic Unit (ALU) to generate essential signals—such as zero, carry, overflow—critical for calculating condition branch outcomes (taken/not taken) during program execution.



## Instruction Types and Formats

The Instruction Set Architecture (ISA) features four distinct instruction formats: R-type, I-type, J-type, and S-type. These formats share a common 6-bit opcode field that determines the specific operation of the instruction.

### R-Type (Register Type):

- Opcode (6 bits)
- Rd (4 bits) - Destination register
- Rs1 (4 bits) - First source register
- Rs2 (4 bits) - Second source register
- Unused (14 bits)

 


Figure 1: R-Type Format

### I-Type (Immediate Type):

- Opcode (6 bits)
- Rd (4 bits) - Destination register
- Rs1 (4 bits) - First source register
- Immediate (16 bits) - Unsigned for logic instructions, signed otherwise
- Mode (2 bits) - Used with load/store instructions
- 00: No increment/decrement of the base register
- 01: Post increment the base register (e.g., LW.POI)
- 10-11: Unused


 


Figure 2: I-Type Format

### J-Type (Jump Type):

- Opcode (6 bits)
- Jump Offset (26 bits)
- jmp L: Unconditional jump to target L

- call F: Call function F, pushing return address on the stack
- ret: Return from a function, next PC is the top element of the stack

 

*Figure 3: J-Type Format*

### **S-Type (Stack):**

- Opcode (6 bits)
- Rd (4 bits)
- Unused (22 bits)
- push Rd: Push the value of Rd onto the top of the stack
- pop Rd: Pop the stack and store the topmost element in Rd



*Figure 4: S-Type Format*

## Instruction Set

The figure below shows the instructions supported by this instruction set, with their meaning and decoding.

No.	Instr	Meaning	Opcode Value
<b>R-Type Instructions</b>			
1	AND	$\text{Reg(Rd)} = \text{Reg(Rs1)} \& \text{Reg(Rs2)}$	000000
2	ADD	$\text{Reg(Rd)} = \text{Reg(Rs1)} + \text{Reg(Rs2)}$	000001
3	SUB	$\text{Reg(Rd)} = \text{Reg(Rs1)} - \text{Reg(Rs2)}$	000010
<b>I-Type Instructions</b>			
4	ANDI	$\text{Reg(Rd)} = \text{Reg(Rs1)} \& \text{Imm}^{16}$	000011
5	ADDI	$\text{Reg(Rd)} = \text{Reg(Rs1)} + \text{Imm}^{16}$	000100
6	LW	$\text{Reg(Rd)} = \text{Mem}(\text{Reg(Rs1)} + \text{Imm}^{16})$	000101
7	LW.POI	$\text{Reg(Rd)} = \text{Mem}(\text{Reg(Rs1)} + \text{Imm}^{16})$ $\text{Reg[Rs1]} = \text{Reg[Rs1]} + 1$	000110
8	SW	$\text{Mem}(\text{Reg(Rs1)} + \text{Imm}^{16}) = \text{Reg(Rd)}$	000111
9	BGT	if ( $\text{Reg(Rd)} > \text{Reg(Rs1)}$ ) Next PC = PC + sign_extended ( $\text{Imm}^{16}$ ) else PC = PC + 1	001000
10	BLT	if ( $\text{Reg(Rd)} < \text{Reg(Rs1)}$ ) Next PC = PC + sign_extended ( $\text{Imm}^{16}$ ) else PC = PC + 1	001001
11	BEQ	if ( $\text{Reg(Rd)} == \text{Reg(Rs1)}$ ) Next PC = PC + sign_extended ( $\text{Imm}^{16}$ ) else PC = PC + 1	001010
12	BNE	if ( $\text{Reg(Rd)} != \text{Reg(Rs1)}$ ) Next PC = PC + sign_extended ( $\text{Imm}^{16}$ ) else PC = PC + 1	001011
<b>J-Type Instructions</b>			
13	JMP	Next PC = {PC[31:26], Immediate <sup>26</sup> }	001100
14	CALL	Next PC = {PC[31:26], Immediate <sup>26</sup> }	001101
15	RET	Next PC = top of the stack	001110
<b>S-Type Instructions</b>			
16	PUSH	Rd is pushed on the top of the stack	001111
17	POP	The top element of the stack is popped, and it is stored in the Rd register	010000

Figure 5:Instruction Set

## Data Path Design and details and description

The first step in designing a data path for a computer's microarchitecture is to create a Register Transfer Level (RTL) description for each instruction. This RTL description should determine the required Functional Units (FUs) and the necessary buses for each instruction.

➤ RTL for R-types Instructions:

$$IR \leftarrow \text{Mem}[PC]$$
$$\text{Data1} \leftarrow \text{Reg}[\text{Rs1}]$$
$$\text{Data2} \leftarrow \text{Reg}[\text{Rs2}]$$
$$\text{Alu\_res} \leftarrow \text{funct}(\text{data1}, \text{data2})$$
$$\text{Reg}[\text{Rd}] \leftarrow \text{alu\_res}$$
$$PC \leftarrow PC+1$$

Where  $\text{funct}$  is and operation when the operation is AND and addition when the operation is ADD and subtraction when the operation is SUB.

➤ RTL for ANDI, ADDI(I-type):

$$IR \leftarrow \text{MEM}[PC]$$
$$\text{data1} \leftarrow \text{Reg}(\text{Rs1})$$
$$\text{data2} \leftarrow \text{Extend}(\text{imm16})$$
$$\text{ALU\_result} \leftarrow \text{op}(\text{data1}, \text{data2})$$
$$\text{Reg}(\text{Rd}) \leftarrow \text{ALU\_result}$$
$$PC \leftarrow PC + 4$$

Where the operation is and when opcode is ANDI and addition when opcode is ADDI.

- RTL for I-type: **LW** instruction

$IR \leftarrow MEM[PC]$

$Base \leftarrow Reg(Rs1)$

$Address \leftarrow base + sign\_extend(imm16)$

$Data \leftarrow MEM[address]$

$Reg(Rd) \leftarrow data$

$PC \leftarrow PC + 1$

- RTL for I-type: **SW** instruction

$IR \leftarrow MEM[PC]$

$Base \leftarrow Reg(Rs1)$

$Address \leftarrow base + sign\_extend(imm16)$

$MEM[address] \leftarrow Reg(Rd)$

$PC \leftarrow PC + 1$

- RTL for I-type: **LW.POI** instruction

$IR \leftarrow MEM[PC]$

$base \leftarrow Reg(Rs1)$

$address \leftarrow base + sign\_extend(imm16)$

$data \leftarrow MEM[address]$

$Reg(Rd) \leftarrow data$

$Reg(Rs1) \leftarrow Reg(Rs1) + 1$

$PC \leftarrow PC + 1$

➤ RTL for (I-type) Branch (BEQ)

$IR \leftarrow MEM[PC]$

$data1 \leftarrow Reg(Rs1), data2 \leftarrow Reg(Rd)$

$zero \leftarrow subtract(data1, data2)$

if (zero)  $PC \leftarrow PC + sign\_ext(offset16)$

else  $PC \leftarrow PC + 1$

➤ RTL for (I-type) Branch (BNE)

$IR \leftarrow MEM[PC]$

$data1 \leftarrow Reg(Rs1), data2 \leftarrow Reg(Rd)$

$zero \leftarrow subtract(data1, data2)$

if (! zero):  $PC \leftarrow PC + sign\_ext(offset16)$

else  $PC \leftarrow PC + 1$

➤ RTL for (I-type) Branch (BGT)

$IR \leftarrow MEM[PC]$

$data1 \leftarrow Reg(Rs1), data2 \leftarrow Reg(Rd)$

$zero \leftarrow subtract(data1, data2)$

if (N! = V):  $PC \leftarrow PC + sign\_ext(offset16)$

else  $PC \leftarrow PC + 1$

➤ RTL for (I-type) Branch (BLT)

$IR \leftarrow MEM[PC]$

$data1 \leftarrow Reg(Rs1), data2 \leftarrow Reg(Rd)$

$zero \leftarrow subtract(data1, data2)$

if (! Z && N == V):  $PC \leftarrow PC + sign\_ext(offset16)$

else  $PC \leftarrow PC + 1$

➤ RTL for (J-type) JMP

$Instruction \leftarrow MEM[PC]$

$target \leftarrow PC[31:26] \parallel address26$

$PC \leftarrow target$

➤ RTL for (S-type) CALL

$Instruction \leftarrow MEM[PC]$

$target \leftarrow PC[31:26], Immediate26$

Push ( $PC + 1$ )

$PC \leftarrow target$

➤ RTL for (S-type) RET

$Instruction \leftarrow MEM[PC]$

$PC \leftarrow \text{Top of the stack}$

### Functional Units needed in data path:

- 1- **Instruction memory:** It stores the machine instructions that the CPU fetches and executes, playing a fundamental role in program execution and overall system performance, word addressable with size 4GB.
- 2- **Register File:** with 16 32-bit general-purpose registers: from R0 to R15.
- 3- **ALU:** It performs arithmetic and logical operations, such as addition, subtraction, AND, OR, and more, essential for executing instructions and processing data within the computer.
- 4- **Data memory:** includes a stack allocated as part of its structure, where each cell has a size of 32 bits (one word)
- 5- **Extender:** The extender is a component that is used to expand the width of data from 16 bits to 32 bits, and it can support both signed and unsigned data representations.

### Instruction and Data memory

The memories in the implementation are separated into two parts, instruction memory, and data memory. This was done to solve some conflicts, such as, one instruction might be fetching the instruction from the memory and the other instruction is loading/storing some data from/to the memory, so in order to obey the isolation principle, they need to be separated into different memory elements.

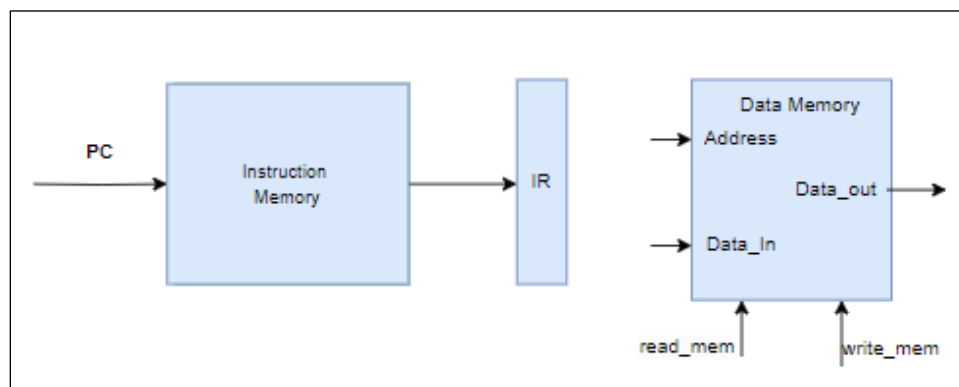


Figure 6 instruction and data memory

The input to the instruction memory is the PC, which is used to fetch and store instructions in the IP register. Conversely, the Data memory has two inputs, namely address and data\_in. These inputs are managed by control units generated by the Main Control Unit.



## Code and Test bench for Data memory:

```

parameter data_mem_size = 1024 ;

module Data_mem (
    input clk,
    input [31:0] address,
    input [31:0] data_in,
    output reg [31:0] data_out,
    input mem_read, // signal for reading from memory
    input mem_write // signal for writing on memory
);

reg [31:0] mem[0:data_mem_size - 1];

always @(posedge clk ) begin

    if (mem_write)
        mem[address] = data_in;

    else if (mem_read)
        data_out = mem[address];

end

initial begin

    // initialize the memory with temporary value.
    for (int i = 0; i < 256; i = i + 1) begin
        mem[i] <= 32'hAAAAAAAA;
        mem[9] <= 32'h99999999;
        mem[8] <= 32'h88888888;
    end

end

end

module Data_mem_tb;
// Inputs
reg clk;
reg [31:0] address;
reg [31:0] data_in;
reg mem_read;
reg mem_write;
wire [31:0] data_out;
Data_mem uut (
    .clk(clk),
    .address(address),
    .data_in(data_in),
    .data_out(data_out),
    .mem_read(mem_read),
    .mem_write(mem_write)
);
always #20 clk = ~clk;
initial begin
    // Initialize Inputs
    clk = 0;
    address = 0;
    data_in = 0;
    mem_read = 0;
    mem_write = 0;
    // Wait for global reset
    #50
    // Test Case 1: Write to Memory
    address = 10;
    data_in = 32'h12345678;
    mem_write = 1;
    mem_read=0;

    #50;
    mem_write = 0;
    mem_read=1;
    #20;
    // Test Case 2: Read from Memory
    mem_read = 1;
    #20;
    #20;
    $finish;
end

```

Figure 7 code and test bench for Data Memory

## Test Bench Result:

 


Figure 8 waveform simulation for Data Memory

Read and Write operations done in the positive edge clock.

## Code and Test bench for Instruction memory:

```

module Inst_mem(
    input [31:0] address,
    output reg [31:0] inst
);

parameter MEM_SIZE = 1024;
parameter WORD_SIZE = 32;

reg [WORD_SIZE-1:0] mem [0:MEM_SIZE-1];

initial begin
    |
    mem[0] = 32'b00111110010000000000000000000000; // PUSH R9 (Push the value of R9 on the
    mem[1] = 32'b01000000000000000000000000000000; // POP R0 (Pop the value on top of the
    mem[2] = 32'b00000100010000001000000000000000; // ADD R1, R0, R2
    mem[3] = 32'h0044001B; // andi $5,$1,6 (I-Type)
    mem[4] = 32'h1E540043; //SW $9,$5,16 (unused mode bits 11) mem[
    /*
    mem[0] = 32'b00111110010000000000000000000000; // PUSH R9 (Push the value of R9 on the
    mem[1] = 32'b01000000000000000000000000000000; // POP R0 (Pop the value on top of the
    mem[2] = 32'b00000100010000001000000000000000; // ADD R1, R0, R2
    mem[3] = 32'h19C40021; // LW R6,R3,4 (Load mem(R1 + sign_
    mem[4] = 32'h158C0010; // LW R6,R3,4
    mem[5] = 32'h090C8000; // sub R4,R3,R2
    mem[6] = 32'h0D44001B; // andi $5,$1,6 (I-Type)
    mem[7] = 32'h1E540043; //SW $9,$5,16 (unused mode bits 11) mem[RS+]
    mem[9] = 32'h34000004; // CALL 4 (Pushes PC+1 to the top of the stack
    mem[9] = 32'h38000000; // RET (return PC to the value stored on top of the
    mem[10] = 32'h33FFFFFFD; // JMP -3 (constant represented in 2's com
    */

end

always @(address) begin
    inst <= mem[address];
end
endmodule

```

Figure 9 code and test bench for instruction memory

## Test Bench Result:

Signal name	Value	20	40	60	80	100	120
<b>addr</b>	00000005	00000000	00000001	00000002	00000003	00000004	00000005
<b>data_out</b>	xxxxxxx	3E400000	40000000	04408000	0D44001B	1E540043	xxxxxxx

Figure 10 test bench for instruction memory

## ALU:

In addition to performing arithmetic and logical operations, the Arithmetic Logic Unit (ALU) also plays a crucial role in setting flags that help control the flow of program execution and make decisions in a computer's central processing unit (CPU). These flags typically include the Zero Flag (Z), Carry Flag (C), Overflow Flag (V), and Sign Flag (S). The Zero Flag is set when the result of an operation is zero, the Carry Flag helps manage carry or borrow during addition and subtraction, the Overflow Flag signals when arithmetic overflow occurs, and the Sign Flag represents the sign of the result (positive or negative). These flags are used in conditional branching and decision-making instructions, allowing the CPU to respond to different conditions and perform various actions based on the results of ALU operations.

 


Figure 11 ALU

## Code and Test bench for ALU:

```
module ALU(
    input [1:0] alu_op,
    input [31:0] data1,
    input [31:0] data2,
    output reg [31:0] alu_res,
    output reg C,
    output wire N, V, Z // negative, overflow, and zero
);

always @(*) begin
    case (alu_op)
        2'b00: {C, alu_res} = data1 + data2;
        2'b01: {C, alu_res} = data1 - data2;
        2'b10: {C, alu_res} = data1 & data2;
    endcase
end

assign Z = ~(|alu_res); // Zero flag
assign V = (alu_res[31] ^ C); // Overflow flag
assign N = alu_res[31]; // Negative flag
endmodule

module alu_tb;
    // Signals
    reg [1:0] alu_op;
    reg [31:0] a, b;
    wire [31:0] out;
    wire C, N, V, Z;
    // Instantiate ALU module
    ALU uut (
        .alu_op(alu_op),
        .data1(a),
        .data2(b),
        .alu_res(out),
        .C(C),
        .N(N),
        .V(V),
        .Z(Z)
    );
    initial begin
        a = 32'h0000000A; // 10 in hexadecimal
        b = 32'h00000005; // 5 in hexadecimal
        alu_op = 2'b00; // Addition
        #10;
        $display("a = %h, b = %h, operation = %h, out = %h", a, b, alu_op, out);
        alu_op = 2'b01; // Subtraction
        #10;
        $display("a = %h, b = %h, operation = %h, out = %h", a, b, alu_op, out);
        a = 32'h00001112;
        b = 32'h00000004;
        alu_op = 2'b10; // AND
        #10;
        $display("a = %h, b = %h, operation = %h, out = %h", a, b, alu_op, out);
        $finish;
    end
endmodule
```

Figure 12 code and test bench for ALU

## Test Bench Result:

Signal name	Value	4	8	12	16	20	24	28
alu_op	2	0		1		2		
a	00001112		0000000A			00001112		
b	00000004		00000005			00000004		
out	00000000	0000000F		00000005		00000000		
C	0							
N	0							
V	0							
Z	1							

Figure 13 ALU test-bench

## Register File

Register File architecture within a computer system. It comprises three registers: RA, RB, and RW, each with a 4-bit width. These registers are connected to two primary data buses, BusA and BusB, both of which have a width of 32 bits. This architecture enables reading from and writing to these registers through BusW2 and BusW1 when their signal values one.

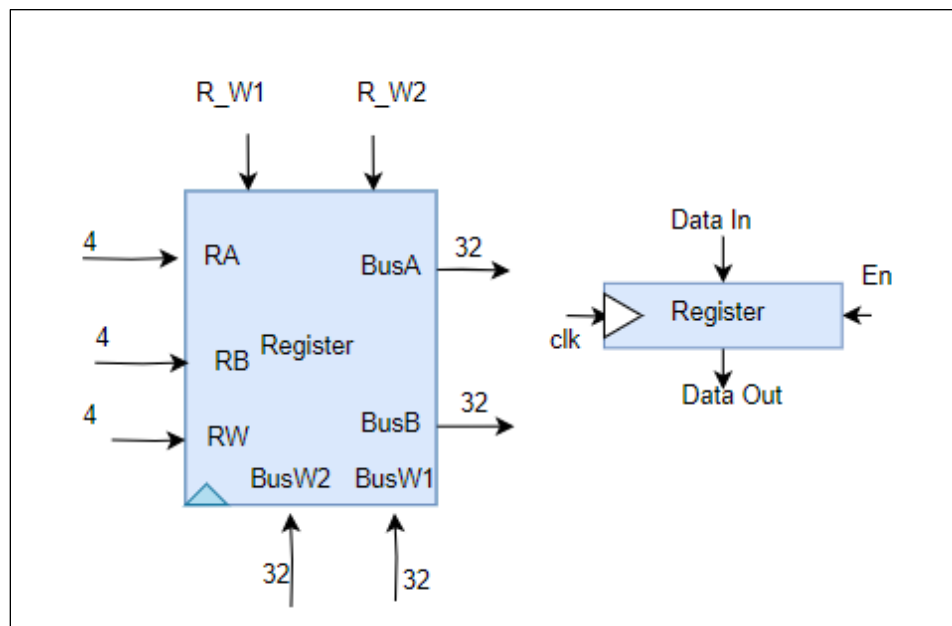


Figure 14 Register file

## Code and Test bench for Register File:

```

module register_file(
    input clk,
    input [3:0] RA_address,
    input [3:0] RB_address,
    input [3:0] RW_address,
    input [31:0] busW1,
    input [31:0] busW2,
    output reg [31:0] busA,
    output reg [31:0] busB,
    input reg_write1,
    input reg_write2
);

reg [31:0] regs [15:0];

always @(posedge clk) begin

    busB <= regs[RB_address];
    busA <= regs[RA_address];

    if (reg_write1) begin
        regs[RW_address] <= busW1;
    end

    if (reg_write2) begin
        regs[RA_address] <= busW2;
    end

end

initial begin

    regs[0] <= 32'h00000000;
    regs[1] <= 32'h00000001;
    regs[2] <= 32'h00000002;
    regs[3] <= 32'h00000003;
    regs[4] <= 32'h00000004;
    regs[5] <= 32'h00000005;
    regs[6] <= 32'h00000006;
    regs[7] <= 32'h00000007;
    regs[8] <= 32'h00000008;
    regs[9] <= 32'h00000009;
    regs[10] <= 32'h0000000A;
    regs[11] <= data_mem_size;

end

endmodule

```

```

module register_file_tb;

// Inputs
reg clk;
reg [3:0] RA_address;
reg [3:0] RB_address;
reg [3:0] RW_address;
reg [31:0] busW1;
reg [31:0] busW2;
reg reg_write1;
reg reg_write2;

// Outputs
wire [31:0] busA;
wire [31:0] busB;

// Instantiate the Unit Under Test (UUT)
register_file uut (
    .clkToUtk,
    .RA_address(RA_address),
    .RB_address(RB_address),
    .RW_address(RW_address),
    .busW1(busW1),
    .busW2(busW2),
    .busA(busA),
    .busB(busB),
    .reg_write1(reg_write1),
    .reg_write2(reg_write2)
);

// Clock generation
always #10 clk = ~clk;

// Test procedure
initial begin
    // Initialize Inputs
    clk = 0;
    RA_address = 0;
    RB_address = 0;
    RW_address = 0;
    busW1 = 0;
    busW2 = 0;
    reg_write1 = 0;
    reg_write2 = 0;

    // Wait 100 ns for global reset to finish
    #50;

    // Add stimulus here
    // Example: Writing to a register and reading from it
    reg_write1 = 1;
    RW_address = 4;
    busW1 = 32'hA5A5A5A5;
    #20;
    reg_write1 = 0;
    RA_address = 4;

```

Figure 15 code and test bench for Register File

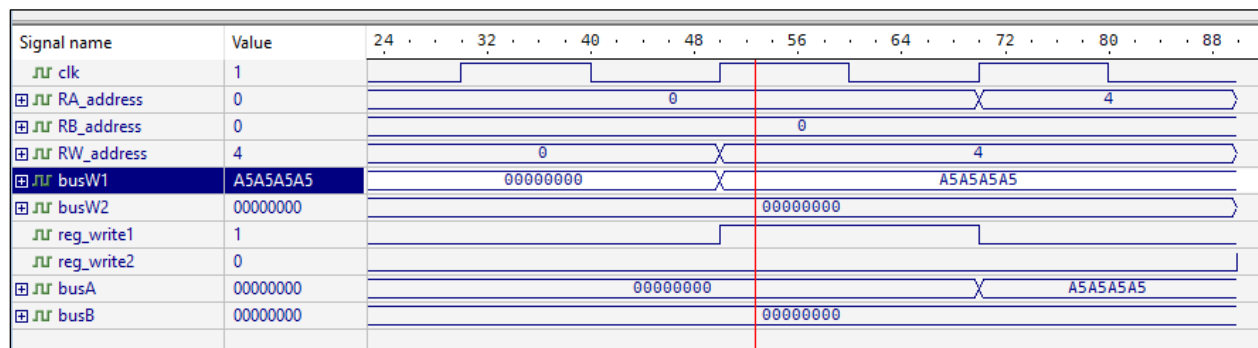


Figure 16 Register File wave form

## Extenders

The extender is versatile in that it can support both signed and unsigned data representations. This implies that it can handle data values that are interpreted as either signed integers (with a sign bit) or unsigned integers (without a sign bit). Depending on the specific implementation and configuration, the extender would appropriately sign-extend or zero-extend the 16-bit input to a 32-bit output.

- Sign-extension for signed data: If the 16-bit input represents signed data, the extender would copy the sign bit (the most significant bit) to fill the additional 16 bits to create a valid 32-bit signed value.
- Zero-extension for unsigned data: If the 16-bit input represents unsigned data, the extender would simply pad the lower 16 bits with zeros to create a 32-bit unsigned value.

 


Figure 17 Extender

## Code and Test bench for Extender:

```
module extender(
    input [15:0] A,
    output reg [31:0] B,
    input extend_op
);

always @(*) begin
    if (extend_op == 0)
        B <= {16'b0, A[15:0]}; // unsigned immedia
    else
        B <= {{16{A[15]}}, A[15:0]}; // signed ext
end

module extender_tb;
    // Inputs
    reg [15:0] A;
    reg extend_op;

    // Outputs
    wire [31:0] B;
    extender uut (
        .A(A),
        .R(R),
        .extend_op(extend_op)
    );

    // Test procedure
    initial begin
        // Initialize Inputs
        A = 0;
        extend_op = 0;

        #10;
        A = 16'h1234;
        extend_op = 0; // Zero extension
        #20;

        // Test Case 3: Sign Extension with negative value
        A = 16'hF234; // MSB is 1, indicating a negative value
        extend_op = 1; // Sign extension
        #20;

        $finish;
    end
endmodule
```

Figure 18 code and test bench for extender

## Test Bench Result:

reg A	1234	1234	29 429 ps	F234
reg extend_op	0			
reg B	00001234	00001234	X	FFFFFF234

Figure 19 simulation for extender

## Multiplexers

A multiplexer is a combinational digital circuit that chooses one of  $2^n$  input lines and feeds it to a single output line based on their values. The number of selection lines, often known as "select lines" or "control lines," specifies how many input lines may be chosen. There are two types of multiplexers used on the Datapath 2x1Mux and 4x1 Mux.

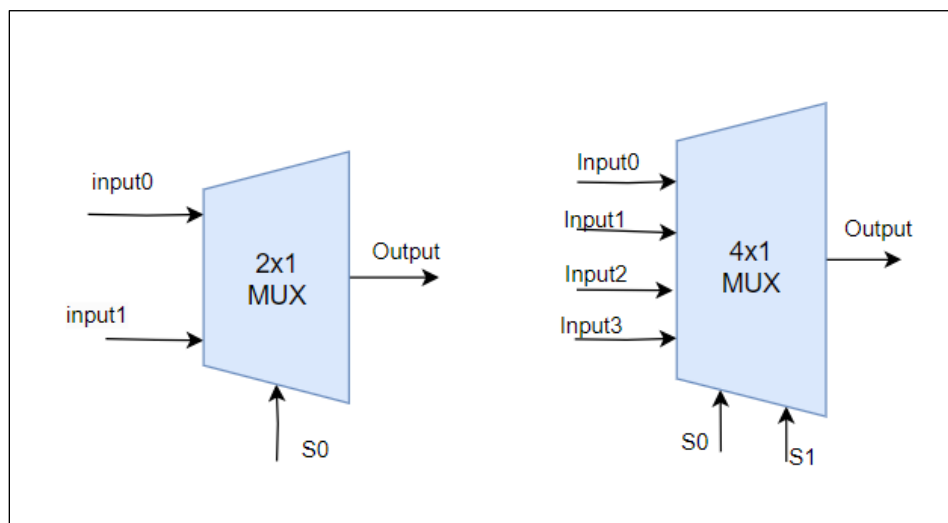


Figure 20 Multiplexers

Six of 2x1Mux used in the data path design:

- 1- The selection of the source register for BusA is determined by the value of "sel\_RA," a control line generated by the main control unit. The multiplexer (MUX) at this stage offers a choice between two possible values: Rs1 and sp\_index, and it selects one of them based on the value of "sel\_RA".
- 2- The selection of the source register for BusB is determined by the value of "sel\_RB," a control line generated by the main control unit. The multiplexer (MUX) at this stage offers a choice between two possible values: Rs2 and Rd and it selects one of them based on the value of "sel\_RB".

- 3- The selection of the alu\_operand2 is made based on the value of "sel\_aluOp." This choice determines whether the second operand for the ALU (Arithmetic Logic Unit) will be either an immediate value or the value from BusB.
- 4- The selection of data to be written on Register file from BusW1, selected from memory data out or ALU result by the signal "write\_back".
- 5- The selection of data to be written on Register file from BusW2, selected from BusA +1 or from BusA value -1 by the signal "sel\_BusW2".
- 6- The selection of the data in for memory is made based on the value of "M\_DIN." This choice determines whether the data in for the Memory will be either an PC+1 or BusB value.

Two of 4x1Mux used in the data path design:

- 1- To select the pc value from four choices branch target address, jump address, PC+1 and the PC value for the RET instruction this done by the "pc\_src" signal.
- 2- To select the address for the memory which has three choices ALU result, SP value and SP-1 value this done by the "sel\_mem\_address".

### Instruction Register and Program counter

IR: 32-bit register stores instructions fetched during the fetch stage.

PC: The Program Counter is a special-purpose register in a CPU (Central Processing Unit) that keeps track of the memory address of the next instruction to be fetched and executed.

 


Figure 21 IR and PC



## State diagram

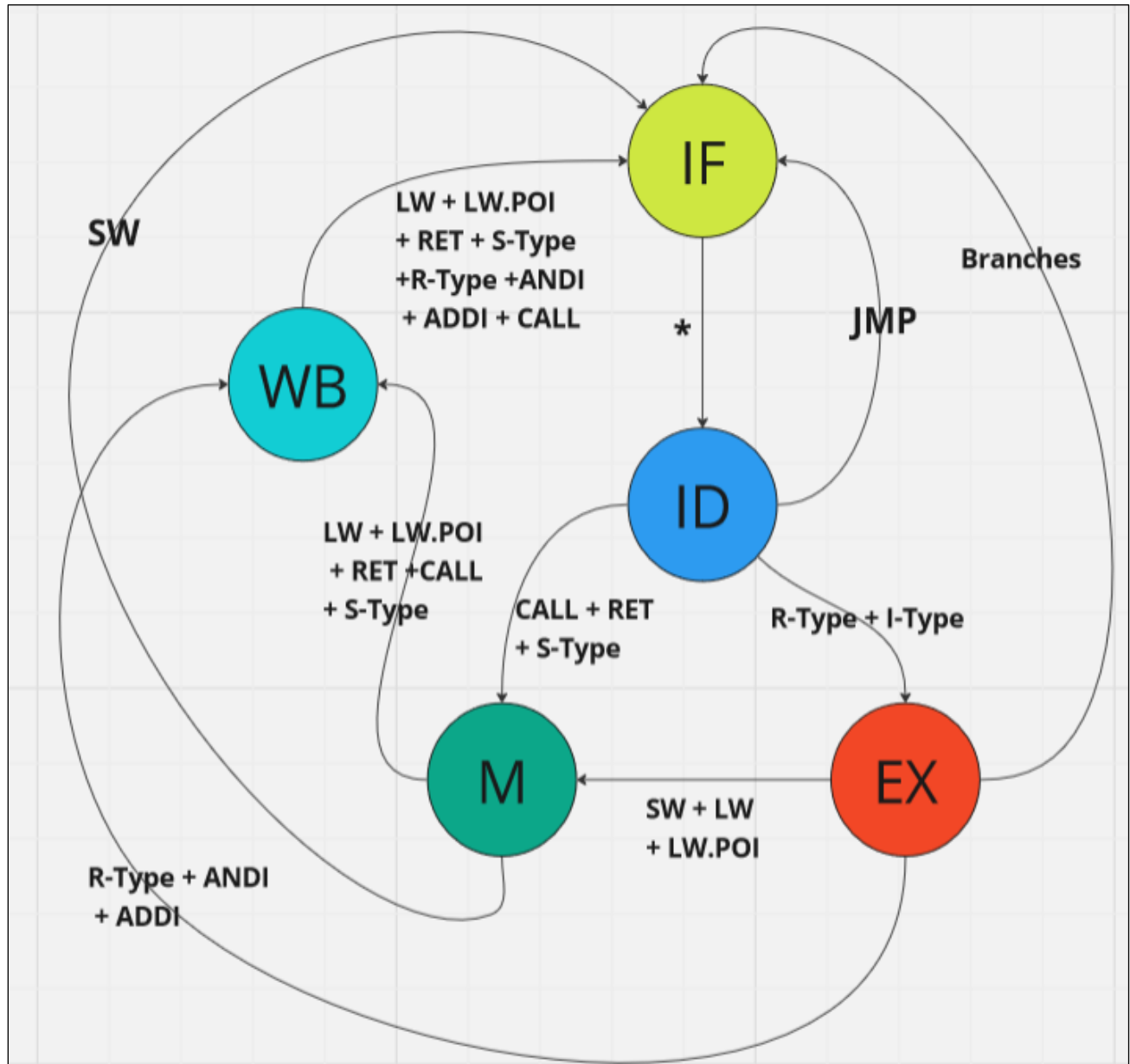


Figure 22: state diagram

## DATA PATH

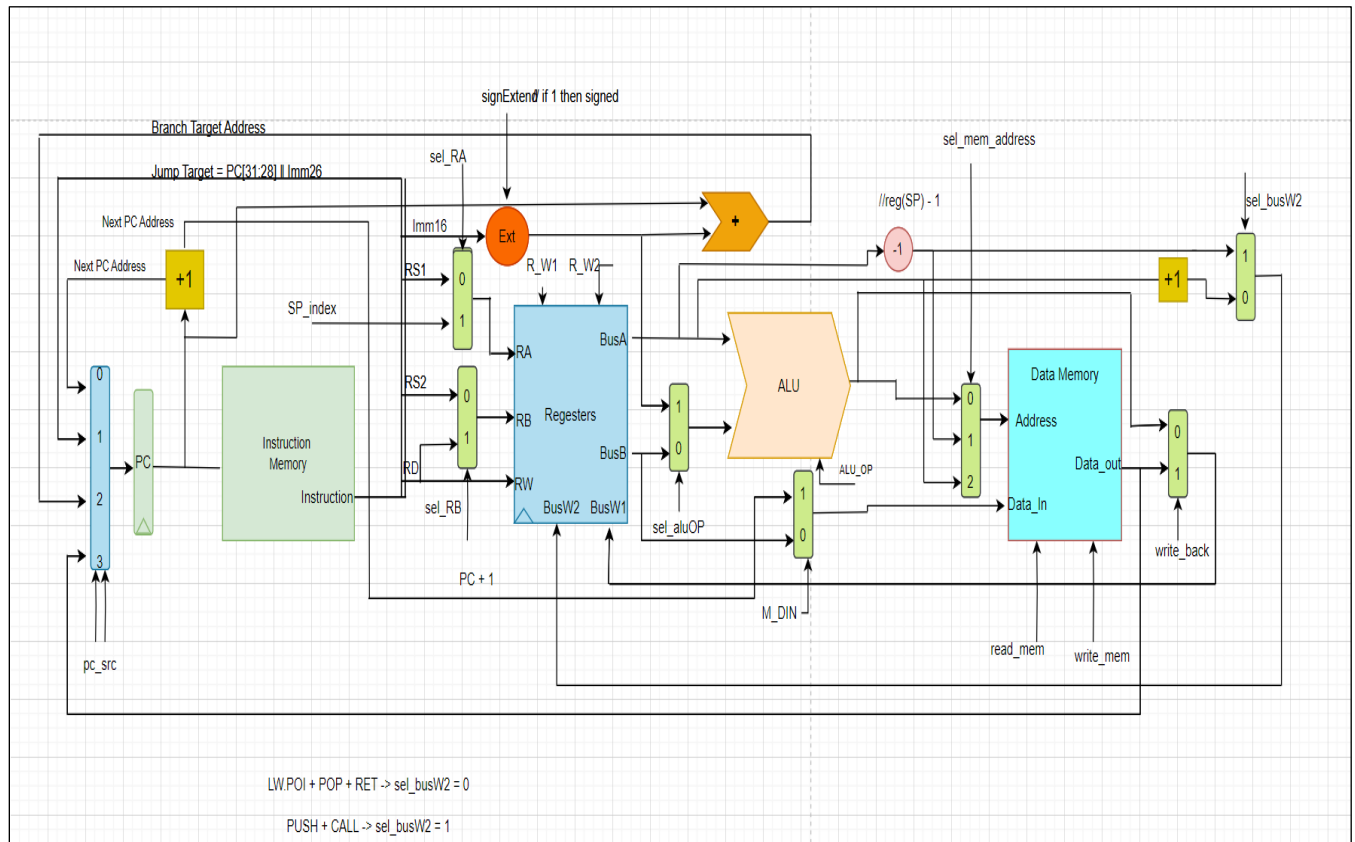


Figure 23: Data Path

## Design Procedure

### Main Control Signals

#### Main Control Input

1. Z (Zero Flag)
2. V (Overflow Flag)
3. C (Carry Flag)
4. N (Negative Flag):
5. opcode [5:0]:
  - 6-bit opcode specifying the type of operation to be performed.

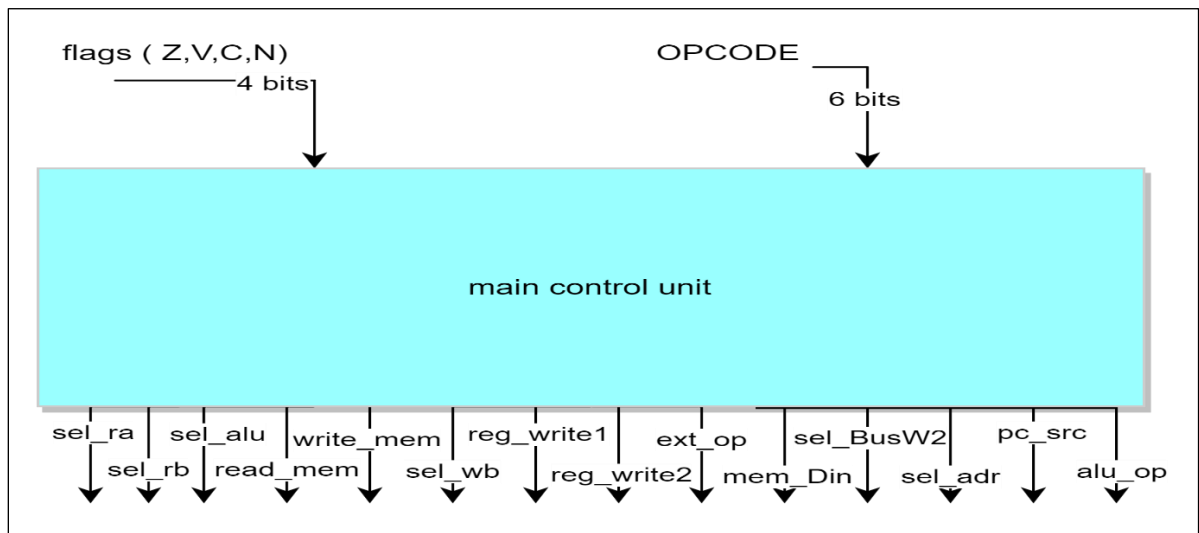


Figure 24: Control Unit

#### Main Control Signals

sel_RA	When 0 → First operand is RS1 (to be read from RF) When 1 → First operand is SP_index(to be read from RF)
sel_RB	When 0 → Second operand is Rs2 (to be read from RF) When 1 → Second Operand is Rd (to be read from RF)

sel_alu_operand	<p>When 0 → Second ALU operand is the value of register (Rs2/Rd) that appears on BusB</p> <p>When 1 → Second ALU operand is the value of the extended 16-bit immediate</p>
sel_address_mem [1:0]	<p>When 00 → The ALU result is the Address to the data memory</p> <p>When 01 → The minus 1 from the value of register RA (SP_INDEX) that appears on BusA is the Address to the data memory</p> <p>When 10 → The value of register RA (SP_INDEX) that appears on BusA is the Address to the data memory</p>
read_mem	<p>When 0 → Data Memory is NOT read</p> <p>When 1 → Data Memory is read: <math>\text{Data\_Out} \leftarrow \text{Memory} [\text{Address}]</math></p>
write_mem	<p>When 0 → Data Memory is NOT written</p> <p>When 1 → Data Memory is written: <math>\text{Mem} [\text{Address}] \leftarrow \text{Data\_in}</math></p>
sel_wb_data	<p>When 0 → The ALU result will be written on the register rd: <math>\text{BusW1} = \text{ALU result}</math></p> <p>When 1 → Data from memory will be written on the register rd: <math>\text{BusW1} = \text{Data\_out}</math></p>
reg_write1	<p>When 0 → no write in the rd Register</p> <p>When 1 → Destination Register Rd is written with the data on BusW1</p>
reg_write2	<p>When 0 → no write in the RA (RS1 OR SP_INDEX) Register</p> <p>When 1 → RA (RS1 OR SP_INDEX) Register is written with the data on BusW2</p>
extend_op	<p>When 0 → 16-bit immediate is Zero-Extended</p> <p>When 1 → 16-bit immediate is Sign-Extended</p>
mem_Din	<p>When 0 → The (data in) to the data memory is pc +1 (when the instruction is call )</p>

	When 1 → The (data in) to the data memory is the value of register (Rs2/Rd) that appears on BusB
sel_BusW2	When 0 → The plus of the Data on the BusA will be written on the register RA (RS1 OR SP_INDEX ),(BusW2 = BusA +1 ) When 0 → The plus of the Data on the BusA will be written on the register RA (RS1 OR SP_INDEX ),(BusW2 = BusA +1 )
alu_op [1:0]	When 00 → ADD operation will be performed in the ALU When 01 → SUB operation will be performed in the ALU When 10 → AND operation will be performed in the ALU

*Table 1: Main Control Signals*

## Main Control Truth Table

R_TYPE	sel_RA	sel_rb	sel_aluOPR	adr_mem	read_mem	write_mem	write_back_data	reg_write1	reg_write2	pc_src	EXT_OP	M_Din	sel_busW2
AND_000000	0	0	0	X	0	0	0	1	0	0	X	x	X
ADD_000001	0	0	0	X	0	0	0	1	0	0	X	x	X
SUB_000010	0	0	0	X	0	0	0	1	0	0	X	x	X
I TYPE INSTRUCTIONS													
ANDI_000011	0	x	1	X	0	0	0	1	0	0	0	x	X
ADDI_000100	0	X	1	X	0	0	0	1	0	0	1	x	X
LW_000101	0	X	1	0	1	0	1	1	0	0	1	x	X
LW.POI_000110	0	X	1	0	1	0	1	1	1	0	1	x	0
SW_000111	0	X	1	0	0	1	X	0	0	0	1	0	X
BGT_001000	0	1	0	X	0	0	X	0	0	(Z==0 && N==V)?2:0	1	x	X
BLT_001001	0	1	0	X	0	0	X	0	0	N!=V?2:0	1	x	X
BEQ_001010	0	1	0	X	0	0	X	0	0	(Z==1)?2	1	x	X
BNE_001011	0	1	0	X	0	0	X	0	0	(Z==0)?2:0	1	x	X

Table 2: Main Control Truth Table

J TYPE INSTRUCTIONS													
JMP 001100	x	x	x	x	0	0	x	0	0	1	1	x	X
CALL 001101	1	x	x	1	0	1	x	0	0	1	1	1	1
RET 001110	1	x	x	2	1	0	0	0	0	3	x	x	0
S TYPE INSTRUCTIONS													
PUSH 001111	1	1	x	1	0	1	0	0	1	0	x	0	1
POP 010000	1	1	x	2	1	0	1	1	1	0	x	x	0

## Logic Equation for Main Control (control\_unit module)

```

module control_unit(
    input Z, V, C, N, // flags, needed for Branch conditions (for PC source signal)
    input [5:0] opcode,
    output reg sel_RA, sel_RB, sel_alu_operand, read_mem, write_mem, sel_wb_data, reg_write1, reg_write2, extend_op, mem_Din, sel_BusW2,
    output reg [1:0] sel_address_mem, pc_src, alu_op
);

    // conditions for LT and GT are swapped here, since it's RD (> < / ==) RS1 (we do RS1 - RD, ...)

    reg branch_taken;
    assign branch_taken = (opcode == BEQ && Z) || (opcode == BNE && !Z) || (opcode == BLT && !Z && N == V) || (opcode == BGT && N != V);
    assign sel_RA = (opcode == CALL || opcode == RET || opcode == PUSH || opcode == POP);
    assign sel_RB = ~(opcode == AND || opcode == ADD || opcode == SUB);
    assign sel_alu_operand = (opcode == ANDI || opcode == ADDI || opcode == LW || opcode == LW_POI || opcode == SW);
    assign sel_address_mem = ( (opcode == RET || opcode == POP) ? 2 : ( opcode == CALL || opcode == PUSH) ? 1 : 0 );
    assign read_mem = (opcode == LW || opcode == LW_POI || opcode == POP || opcode == RET);
    assign write_mem = (opcode == SW || opcode == CALL || opcode == PUSH);
    assign sel_wb_data = (opcode == LW || opcode == LW_POI || opcode == POP);
    assign reg_write1 = (opcode == ADD || opcode == AND || opcode == SUB || opcode == ANDI || opcode == ADDI || opcode == LW || opcode == LW_POI || opcode == POP);
    assign reg_write2 = (opcode == LW_POI || opcode == POP || opcode == PUSH);
    assign extend_op = (opcode != ANDI);
    assign mem_Din = (opcode == CALL);
    assign pc_src = (opcode == JMP || opcode == CALL) ? 1 :
        (opcode == RET) ? 3 :
        (branch_taken) ? 2 : 0;

    assign alu_op = ((opcode == AND || opcode == ANDI) ? 2 : (opcode == SUB || opcode == BEQ || opcode == BLT || opcode == BGT || opcode == BNE) ? 1 : 0);
    assign sel_BusW2 = (opcode == PUSH || opcode == CALL) ? 1 : 0;
    // (opcode == LW_POI || opcode == POP || opcode == RET) ? 0 : 0;

endmodule

```

Figure 25: control unit module

The Test Bench When sets opcode to different values (6'b000000 = AND, 6'b000001 = ADD, 6'b000011 = ANDI, 6'b001000 = BGT)

 


Figure 26: test bench (control unit )

## PC Control Unit

opCode	Z	N	V	PC_src
R_type && ANDI && ADDI&&LW&&LW.POI	X	X	X	0
JMP && CALL	X	X	X	1
BNE	0	X	X	2
BEQ	1	X	X	2
BNE	0	X	X	2
BLT	0	N == V	V == N	2
BGT	X	N != V	V != N	2
RET	X	X	X	3

Table 3: PC\_TABLE

 


Figure 27: PC Source Signal Block





## POP Instruction

### Instruction: POP R0

After Pushing R9 to the stack, we popped the value on top of the stack to R0 to see if the push instruction saved the value of R9 into the memory.

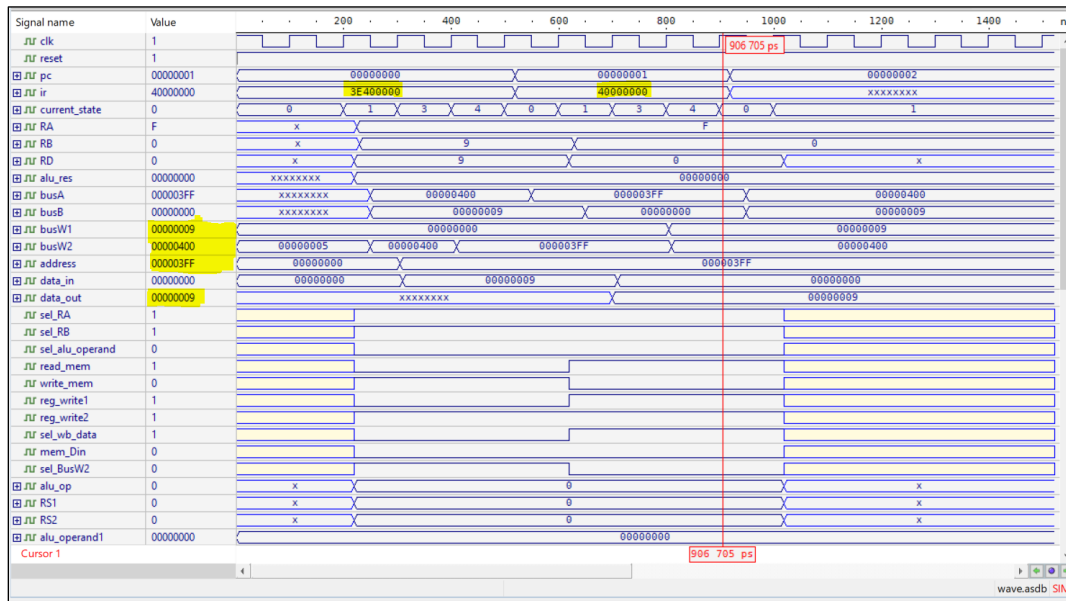


Figure 30 POP

We can see the data\_out is 9, which is the value we popped from the stack (same value we pushed in the previous instruction).

Notice how busW2 is now 0x400 (1024), this value is written as the new value of the stack pointer (it was 1023 before the pop instruction).

Also look at busW1, it holds the value 9, which is the value we pushed to the stack in the previous instruction, this value is written into register R0.

## ADD Instruction

Instruction: ADD R1, R0, R2

R0 holds the value 9, because we popped 9 from top of the stack to R0 – is added with R2 (which holds the value 2).

The result is shown as alu\_res = 0x0B (11 in decimal).

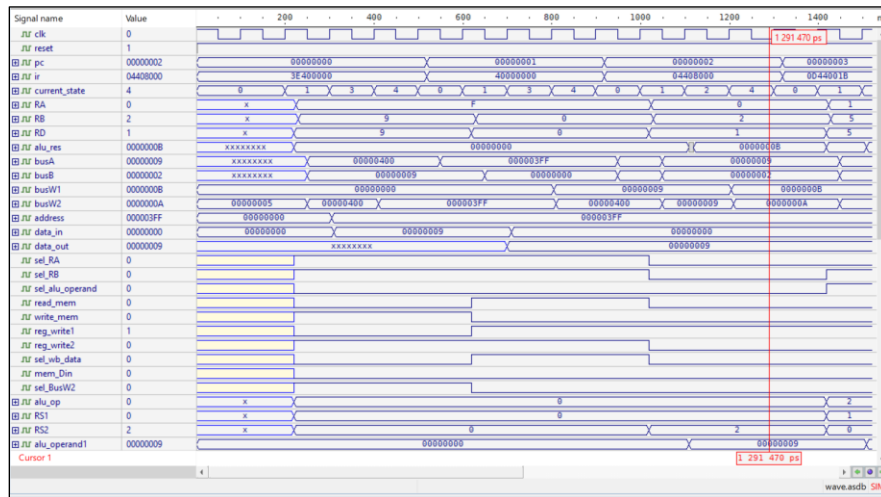


Figure 31 ADD

Notice busW1 which holds the ALU result that will be written to the register R1.

Also look at the signal's values.

## ANDI Instruction

Instruction: ANDI R5, R1, 6

The value of R1 (which is 0xB, the result of the previous instruction) is &-ed with the immediate value 0x06 (alu\_operand2).

See the result in alu\_res = 0x02.

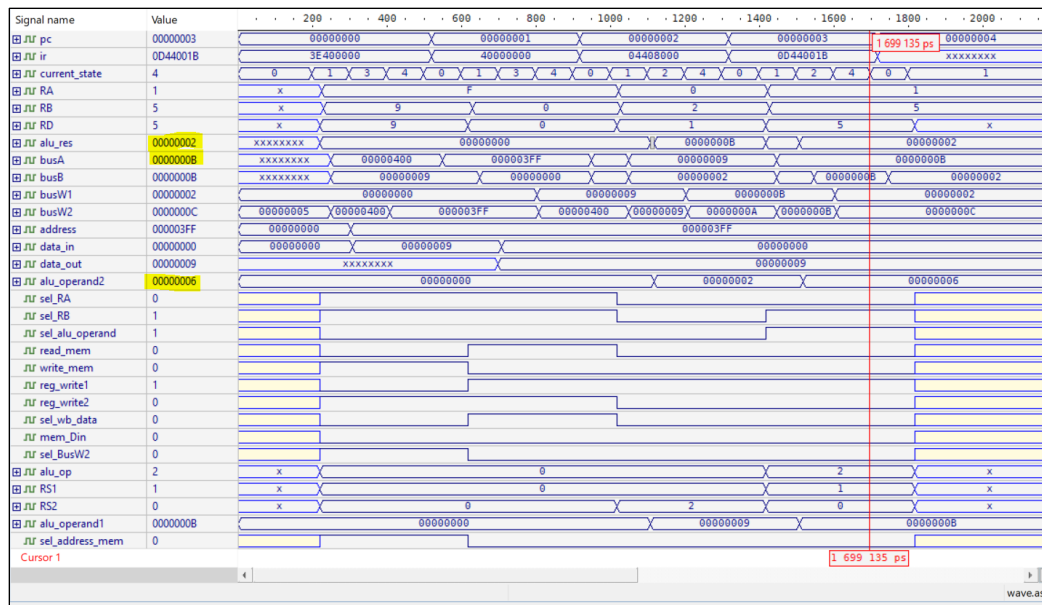


Figure 32 ANDI

## SW Instruction

### Instruction: SW R5, R1, 16

Stores the value in R5 into the memory address ( $R1 + \text{sign\_extend}(16)$ )

busA = 0x0B which is the value in R1 (RA in the diagram), is added with 16 (0x10), the result is 0x1B,

which is the store address. The data\_in is the value of RD, which is 0x02.

 


Figure 33 SW

## LW Instruction

Instruction: LW R6, R3, 0x018

The value stored in the memory address ( $0x018 + R3 = 0x1B$ ) is 2 (from the previous instruction).

This value is loaded into register R6. Notice the values of busW1 and address in the figure below.

 


Figure 34 LW

## LW.POI

Instruction: LW.POI R6, R3, 0x018

The value stored in the memory address ( $0x018 + R3 = 0x1B$ ) is 2 (from the previous store instruction).

The value is loaded into register R6, and the value of R3 is then incremented by 1. Look at busW1 and busW2 (busW1 writes to RD->R6, and busW2 writes to RA->R3).

 


Figure 35 LW.POI

## BGT Instruction

Instruction: BGT R4, R2, -1 (0xFFFF)

Notice that busA holds the value of R2, busA holds the value of R4.

R4 is greater than R2, and we subtracted  $R2 - R4$ , and the result is negative, so the branch is taken.

Note the value on BTA (Branch Target Address), this value will be the next PC value.

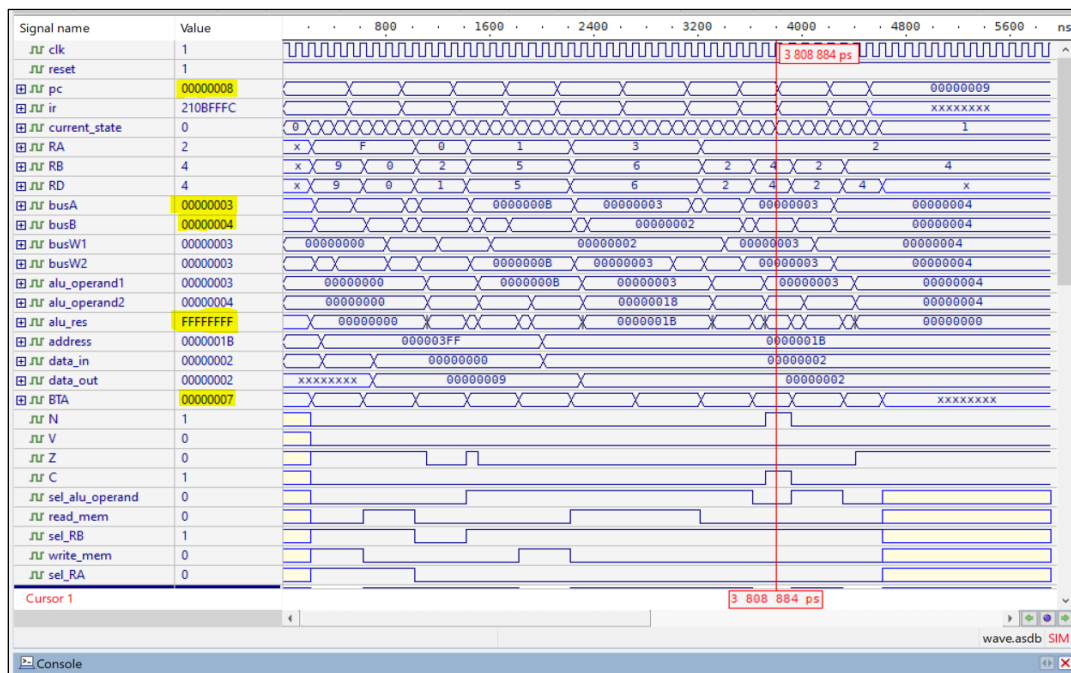


Figure 36 BGT

## CALL Instruction

Instruction: CALL 7 (will go into address 7 in memory)

Notice the value of the next PC in the waveform in the figure below.

The value of PC+1 is shown in data\_in, and it is pushed to the stack in memory address 0x3FF, and the SP is updated from 0x400 (1024) into 0x3FF (1023).

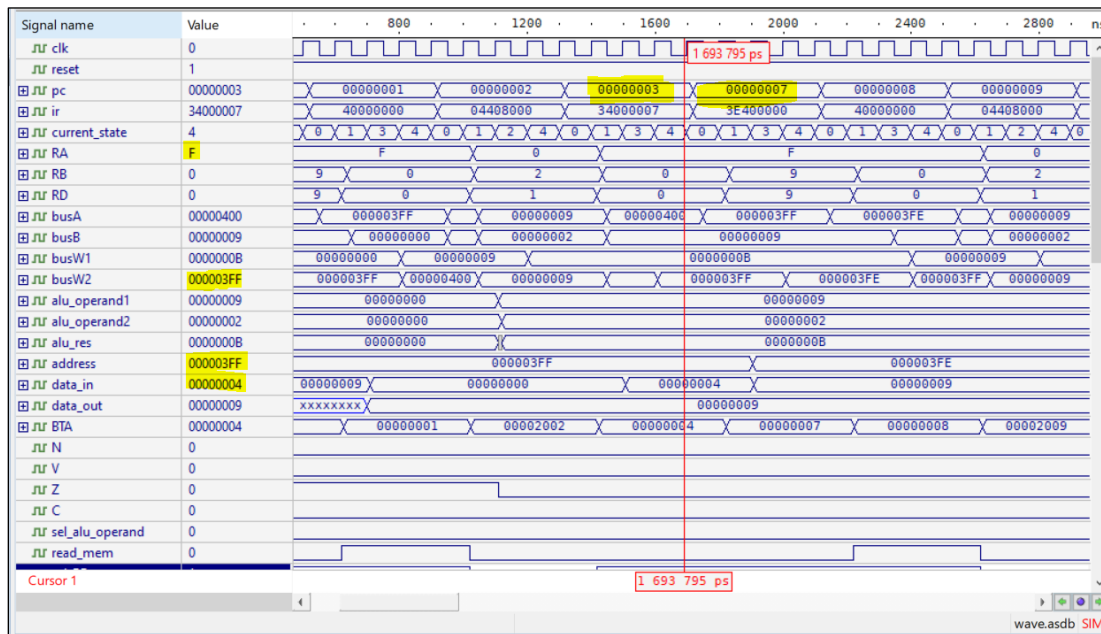


Figure 37 CALL

## RET Instruction

Instruction: RET (set the next PC into the value on top of the stack).

The value on top of the stack is popped from the stack into the PC (notice the next instructions' PC value), and the value of the SP is then incremented by 1 (0x3FF into 0x400).

data\_out = 4 is the value of the next PC, busW2 = 0x400 is the new SP value after pop.

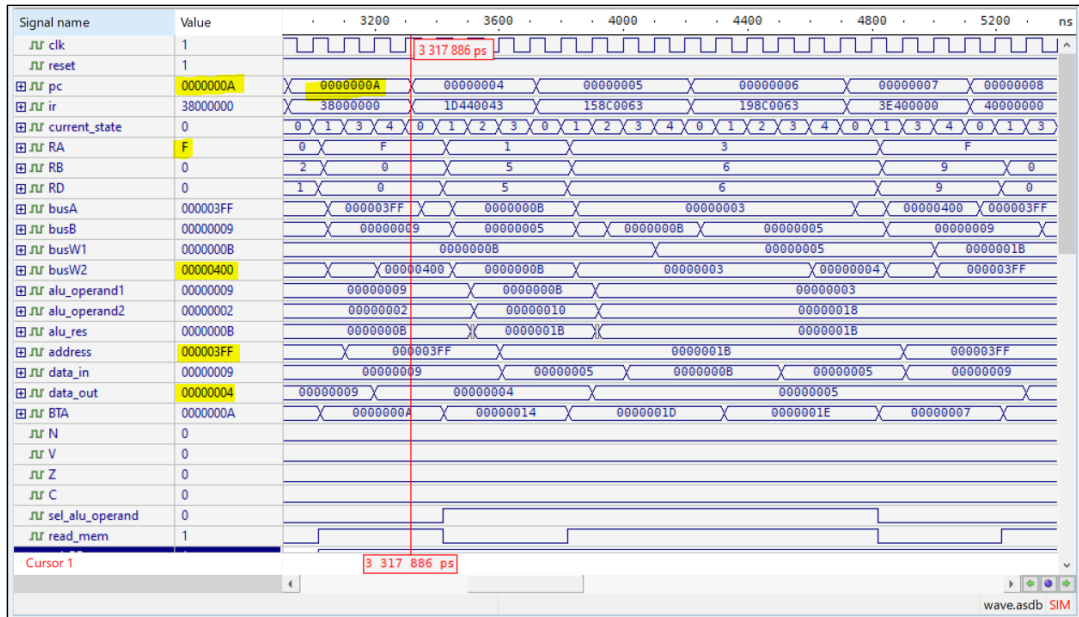


Figure 38 RET



## Team Work

We worked as an integrated team on all parts of the project, from designing to writing the code and finally testing

## Conclusion

The project's objective has been successfully achieved as we completed the design, implementation, and verification of a RISC processor using VERILOG HDL, following a multi-cycle CPU approach. Our methodology involved categorizing instructions that share the same Datapath and subsequently writing the RTL for each group. We carefully derived the components and data transfer from the RTL, specifying all necessary Datapath components. The design process included the development of both the Datapath and Control Unit to ensure the accurate execution of the given instructions. Following the design phase, we implemented each component in VERILOG, conducting individual testing before integrating all components. The final phase involved comprehensive testing of groups of instructions to verify the overall functionality of our design. Remarkably, all instruction groups performed correctly without errors. This project has provided valuable insights into the implementation of a multi-cycle CPU, emphasizing the intricacies of deriving and interconnecting components to realize a specific ISA.